

Figure 1. A Twisted ring counter

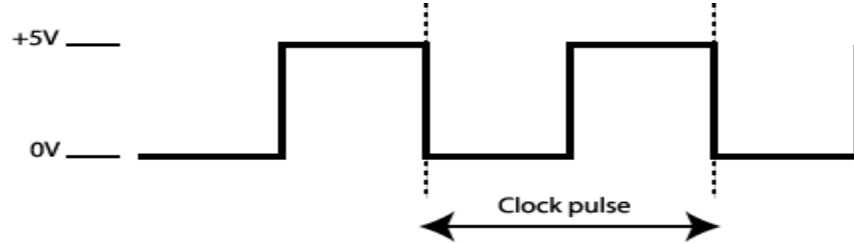


Figure 2. A typical clock signal.

(b) Apply clock pulses (as in Fig 2.) to the circuit and monitor the outputs of the counter (The Q values). What outputs do you get? (show in a table).

(c) In your opinion what is going on in this circuit? Is this circuit a counter? Why or why not?... How many different states can this circuit have when there are N flip flops?

Section 2. The Asynchronous Counter

(a) Connect the circuit for the asynchronous counter as shown in Figure 3. It consists of 3 JK flip-flops with the J and K inputs set to high.

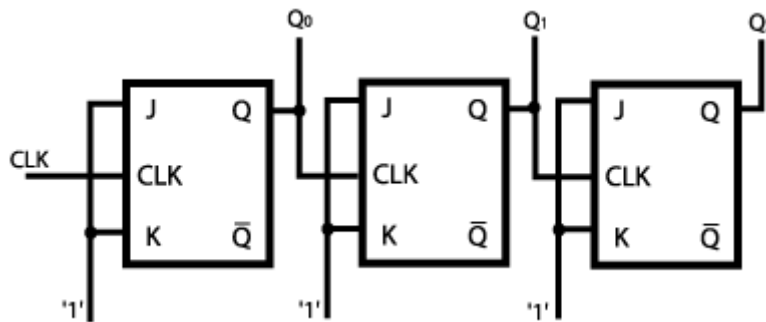


Figure 3. The Asynchronous Counter.

(b) Apply the clock pulses and measure the outputs at the Qn outputs. What values did you observe?

	Q0	Q1	Q2
1			
2			
3			
4			
5			
6			
7			
8			

9			
etc..			

(c) How many states can this counter have for N flip-flops? In your opinion how does this circuit work? What could this circuit be useful for? Why do you think this is called an asynchronous counter, and not a synchronous counter (It has a clock?)?

Section 3. Conclusions

State briefly, but clearly, what you have gained from this laboratory.